# **Finite Computation**

#### I. DEFINING COMPUTATION

Computers are stupid. We need to describe algorithms precisely.

Informal definition of an algorithm: An Algorithm is a set of instructions of how to compute an output from an input by following a sequence of "elementary steps". An algorithm A computes a function F if for every input x, if we follow the instructions of A on the input x, we obtain the output F(x).

#### A. Boolean circuit

**Definition 1 (Boolan circuits)** Let n, m, s be positive integers with  $s \ge m$ . A Boolean circuit with n inputs, m outputs, and s gates, is a labeled directed acyclic graph (DAG) G = (V, E) with s + n vertices satisfying the following properties:

- 1. Exactly n of the vertices have no in-neighbors. These vertices are known as inputs and are labeled with the n labels:  $X[0], \dots, X[n-1]$ .
- 2. The other's vertices are known as gates. Each gate is labeled with  $\land$ ,  $\lor$  and  $\neg$ . Gates labeled with  $\land$  or  $\lor$  have two in-neighbors. Gates labeled with  $\neg$  have one in-neighbor. We will allow parallel edges (and so for example an AND gate can have both its in-neighbors be the same vertex).
- 3. Exactly m of the gates are also labeled with the m labels  $Y[0], \dots, Y[m-1]$  (in addition to their label  $\land, \lor, \lnot$ ). These are known as outputs.

Let  $f:\{0,1\}^n \to \{0,1\}^m$ . We say that the circuit C computes f if for every  $x \in \{0,1\}^n$ , C(x)=f(x).

Briefly speaking, the computation of a Boolean circuit is layer by layer.

**Definition 2 (AON-CIRC Programming language)** An AON-CIRC program is a string of lines of the form foo = AND(bar, blah), foo = OR(bar, blah) and foo = NOT(bar) where foo, bar and blah are variable names. Variables of the form X[i] are known as input variables, and variables of the form Y[j] are known as output variables. In every line, the variables on the righthand side of the assignment operators must either be input variables or variables that have already been assigned a value before.

**Theorem 1 (Equivalence of circuits and straight-line programs)** Let  $f : \{0,1\}^n \to \{0,1\}^m$  and  $s \ge m$  be some number. Then f is computable by a Boolean circuit of s gates if and only if f is computable by an AON-CIRC program of s lines.

### B. The NAND function

**Theorem 2** NAND computes AND, OR, NOT. We can compute AND, OR, and NOT by composing only the NAND function.

```
\begin{split} NOT(a) &= NAND(a, a) \\ AND(a, b) &= NOT(NAND(a, b)) \\ OR(a, b) &= NOT(NOT(NOT(a), NOT(b))) \end{split}
```

**Theorem 3** NAND is a universal operation. For every Boolean circuit C of s gates, there exists a NAND circuit C' of at most 3s gates that computes the same function as C.

Just like we did for Boolean circuits, we can define a programming-language analog of NAND circuits. It is even simpler than the AON-CIRC language since we only have a single operation.

**Theorem 4 (Equivalence of NAND circuits and straight-line programs)** Let  $f: \{0,1\}^n \to \{0,1\}^m$  and  $s \ge m$  be some number. Then f is computable by a NAND circuit of s gates if and only if f is computable by an NAND-CIRC program of s lines.

# II. SYNTACTIC SUGAR, AND COMPUTING EVERY FUNCTION

"syntactic sugar" in programming language: not changing the definition of the language, but merely introducing some convenient notational shortcuts.1 We will use several such "syntactic sugar" constructs to make our descriptions of NAND-CIRC programs shorter and simpler.

### III. SOME EXAMPLES SYNTACTIC SUGAR

- Constants
- Functions / Macros
- Conditional statements: foo = IF(condition, blah, foo)

## IV. THE LOOKUP FUNCTION

**Definition 3 (Lookup function)** For every k, the lookup function  $LOOKUP_k : \{0,1\}^{2^k+k} \to \{0,1\}$  is defined as follows: For every  $x \in \{0,1\}^{2^k}$  and  $i \in \{0,1\}$ ,

$$LOOKUP_k(x,i) = x_i \tag{1}$$

**Theorem 5 (Lookup function)** For every k, there is a NAND-CIRC program that computes the function  $LOOKUP_k$ :  $\{0,1\}^{2^k+k} \to \{0,1\}$ . Moreover, the number of lines in this program is at most  $4 \cdot 2^k$ .

Lemma 1 (Lookup function) For every  $k \geq 2$ ,  $LOOKUP_k(x_0, \dots, x_{2^k-1}, i_0, \dots, i_{k-1})$  is equal to

$$IF(i_0, LOOKUP_k(x_0, \cdots, x_{2^{k-1}-1}, i_1, \cdots, i_{k-1}), LOOKUP_k(x_{2^{k-1}}, \cdots, x_{2^{k}-1}, i_1, \cdots, i_{k-1}))$$
 (2)

### V. COMPUTING EVERY FUNCTION

**Theorem 6 (Universality of NAND)** There exists some constant c > 0 such that for every n, m > 0 and function  $f: \{0,1\}^n \to \{0,1\}^m$ , there is a NAND circuit with at most  $c \cdot m2^n$  gates that computes the function f.